

AN833 APPLICATION NOTE

Connecting pin16 at the rectified mains through a resistor, it is possible to define the modulation depth using the formula:

$$\frac{\Delta f_{sw}}{f_{sw}} = K \frac{V_{IPK} \cdot R_{OSC}}{V_{RMS} \cdot R_{fm}} \Rightarrow R_{fm} = K \cdot \frac{V_{IPK(mains)} \cdot R_{OSC} \cdot f_{sw}}{V_{RMS(pin7)} \cdot \Delta f_{sw}}$$

where:

R_{fm} is the programming current resistor.

K is a constant value = 0.1157


V_{IPK} is the $V_{RMSmAINS} \cdot \sqrt{2}$

V_{RMS} is the voltage at pin 7

Typically a good compromise can be 10% to 20% of the starting frequency. Designing the frequency modulation it is useful to remind few points :

- The switching frequency (f_{sw}) is modulated by the mains instantaneous value and decreases as the rectified voltage increases, so the minimum f_{sw} occurs at the input peak voltage and current (see fig. 2).
- The switching losses increase with the frequency (and obviously with the current).
- The current ripple increases (for the same boost inductor value) as the switching frequency decreases, the higher current ripple produces an higher EMI.

Figure 2. Modulation Frequency Normalized in a Half Cycle of the Mains Voltage. (eg. R_{FM} = 1100kΩ, R_{osc} = 24kΩ, C_{osc} = 820pF).

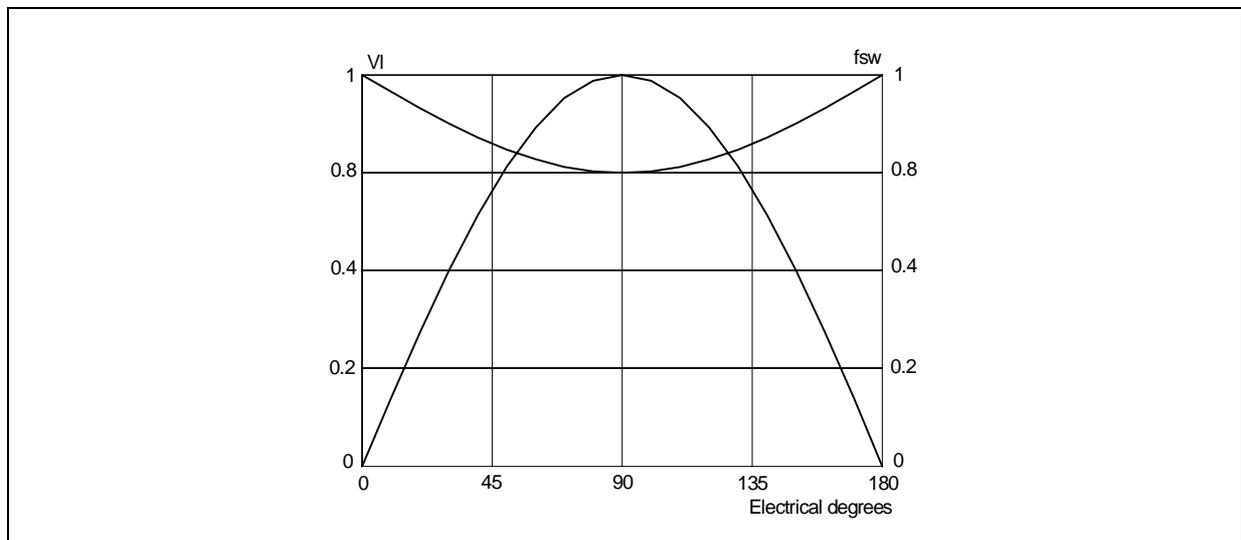

Considering the above mentioned points, to make a reasonable comparison with an equivalent fixed frequency PFC application in terms of EMI, it is recommended to modify the starting frequency (oscillator).

The suggested criterion for designing a L4981B application is to follow the same procedure used for the fixed frequency version (L4981A) except for the oscillator that must be designed for the desired frequency (f_{min}) that occurs at the peak of the current, plus the modulation contribution, that is:

$$f_{sw} = \Delta f_{sw} + f_{min} = \frac{2.44}{R_{OSC} \cdot C_{OSC}}$$

eg. designing a 100kHz minimum fsw with a modulation depth » 20%:

$$f_{sw} = 124\text{KHz} = \frac{2.44}{24 \cdot 10^{-3} \cdot 0.82 \cdot 10^{-9}}$$

In this way the advantage, in terms of reduction of the peak of energy in the noise spectrum, is remarkable. On the other hand the increase of switching losses can be neglected because the maximum frequency occurs at the minimum line current.

Information furnished is believed to be accurate and reliable. However, STMicroelectronics assumes no responsibility for the consequences of use of such information nor for any infringement of patents or other rights of third parties which may result from its use. No license is granted by implication or otherwise under any patent or patent rights of STMicroelectronics. Specifications mentioned in this publication are subject to change without notice. This publication supersedes and replaces all information previously supplied. STMicroelectronics products are not authorized for use as critical components in life support devices or systems without express written approval of STMicroelectronics.

The ST logo is a registered trademark of STMicroelectronics.
All other names are the property of their respective owners

© 2003 STMicroelectronics - All rights reserved

STMicroelectronics GROUP OF COMPANIES

Australia - Belgium - Brazil - Canada - China - Czech Republic - Finland - France - Germany - Hong Kong - India - Israel - Italy - Japan -
Malaysia - Malta - Morocco - Singapore - Spain - Sweden - Switzerland - United Kingdom - United States

www.st.com