
High-side current sensing for applications using high common-mode voltage

Nicolas Aupetit

Introduction

This application note explains how to extend the common input voltage range of a standard operational amplifier (op amp) to realize a high-side current sensing.

When a high-side current measurement is needed, we generally use specific amplifiers from the TSC10x family. These high-side current sensing amplifiers can amplify input differential signals at a common-mode voltage well beyond their power supply rail.

Even if the TSC10x can work with a common-mode voltage largely above its power supply, it is limited to 70 V when using the TSC103.


In this application note, we will see how to overcome this limitation to realize a high-side current sensing simply by using a standard op amp and some external components.

Contents

1	Schematic and description	3
2	Application.....	4
3	Error analysis	6
	3.1 Impact of resistor mismatches.....	6
	3.2 Impact of input voltage offset (V_{io}).....	7
	3.3 Total error.....	8
4	Application measurement.....	9
5	Conclusion.....	10
6	Revision history	11

1 Schematic and description

Figure 1: General system overview

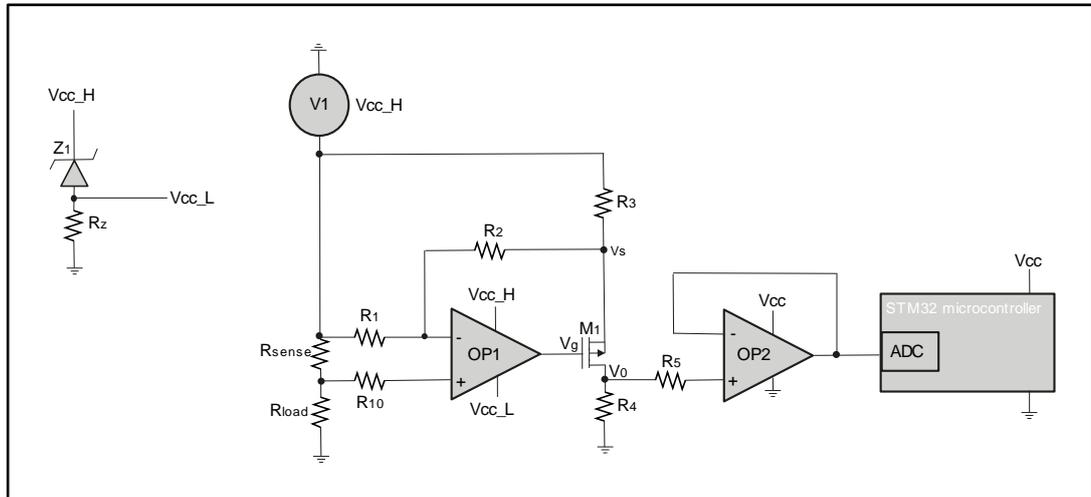

In this application, the power source, V1, works at 150 V. The main goal is to measure the current delivered by V1 thanks to a shunt resistor. To limit power dissipation in the shunt, it's value should be chosen as low as possible. If we follow this procedure, the V_{sense} ($I_{sense} * R_{sense}$) generated through the shunt will also be small. To get a precise measurement for low current, a precision op amp such as the TSZ121 is used. The TSZ121 is a chopper op amp with an extremely low input offset voltage of 8 μV max. over temperature. It is also biased with a very low current of 40 μA .

The measured current value is then treated with a STM32 microcontroller which works with a power supply of 3.3 V. But, the TSZ121 is a 5 V op amp, and in this application the common voltage is up to 150 V.

To use the TSZ121 in its operating condition, i.e. without burning it by applying 150 V on its input, the V1 voltage is used to generate a positive power supply (V_{cc_H}) for the first op amp (OP1). Thanks to a Zener diode, with a 4.7 V breakdown voltage, the negative power supply (V_{cc_L}) of the TSZ121 is generated. In this way the TSZ121 is powered with 4.7 V (in this example, $V_{cc_H} = 150 \text{ V}$ and $V_{cc_L} = 145.3 \text{ V}$).

The resistor, R_z , is used to bias the Zener diode ($\sim 5 \text{ mA}$) and provides a return path for the bias current of the TSZ121 ($\sim 40 \mu\text{A}$).

The voltage, V_{sense} , is the result of the current flowing through R_{sense} , and it is amplified thanks to the resistors R_1 , R_2 , R_3 , and R_4 .

The P-MOSFET, M1, sources an accurate output current proportional to the current flowing into R_{sense} . Then, thanks to the R_4 resistor, M1 generates a voltage, V_o , with respect to ground which is proportional to the high-side current. The voltage output of the first stage, can be given by [Equation 1](#).

Equation 1


$$V_o = \frac{V_{sense} R_4}{R_1 R_3} (R_1 + R_2 + R_3)$$

The second op amp, OP2, is necessary to buffer the V_o voltage. An R_5 resistor may be added to protect the intrinsic protection diode of the OP2 in case a high current flows into the input pins at startup.

2 Application

In this section, we will consider a typical application used to measure the current of an industrial motor control powered with 150 V, as illustrated in [Figure 2](#).

Figure 2: Typical application

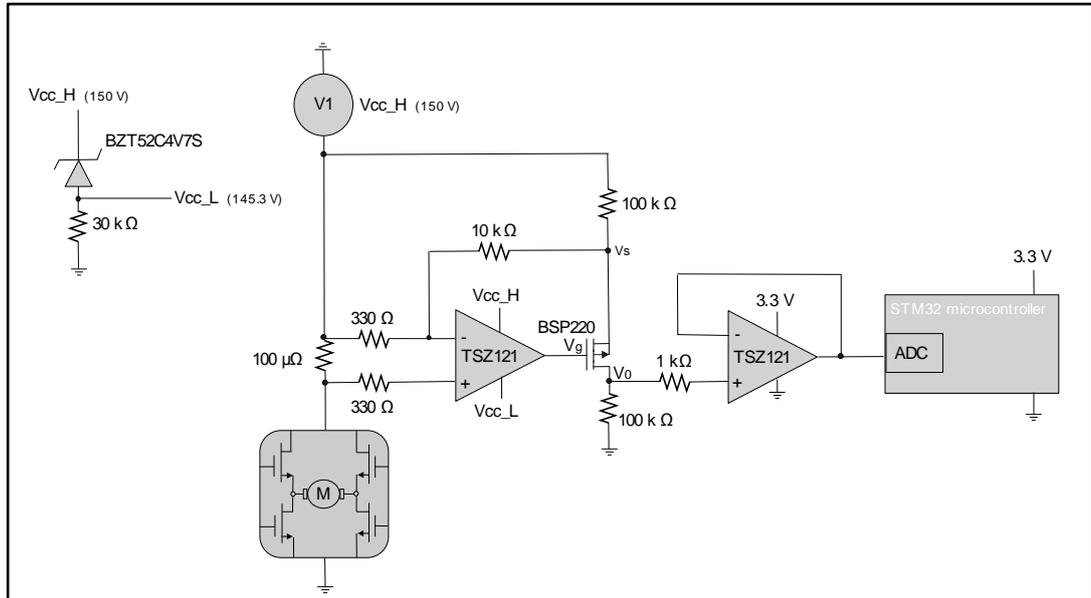

The maximum current drawn by the motor control is 100 A. So, for a 0.1 mΩ shunt resistor, the maximum V_{sense} is 10 mV. The maximum output voltage is dependent on the V_{sense} voltage, and the resulting output current flowing across R_4 . As this current is treated by the ADC of the STM32 microcontroller, the maximum output voltage, V_o , must not exceed 3.3 V.

The gain of the whole system is given by [Equation 2](#).

Equation 2

$$Gain = \frac{V_o}{V_{sense}} = \frac{(R_1 + R_2 + R_3)}{R_1} \cdot \frac{R_4}{R_3}$$

The values of the components must be carefully chosen for the system to work properly.

The main goal is to work with a low $|V_{gs}|$ so as not to saturate the output of OP1. When the current $|I_{ds}|$ increases, $|V_{ds}|$ decreases, so $|V_{gs}|$ must increase while V_s is decreasing. Therefore the gate voltage is limited by the low saturation of OP1 (V_{cc_L}) for a high I_{ds} (see [Equation 3](#)).

Equation 3

$$|V_{gs \max}| < V_s - V_{cc_L}$$

$$|V_{gs \max}| < V_{zener} - \left(1 + \frac{R_2}{R_1}\right) \cdot V_{sense}$$

As keeping I_{ds} low helps the situation, it is better to choose a high value for R_4 .

To avoid any saturation of the op amp output, the gain, relative to OP1 and given by the ratio R_2/R_1 ([Equation 3](#)), should not be too big.

Consequently, there is a compromise to be made regarding the choice of component values (see [Equation 4](#)).

Equation 4

$$|V_{gs \max}| < V_{zener} - \frac{R3 \cdot (R1 + R2)}{R4 \cdot (R1 + R2 + R3)} \cdot V_{o_max}$$

Where V_{gmax} is the V_{gs} needed to allow a current into the transistor of $I_{d_max} = V_{o_max}/R4$ and $V_{zener} = V_{cc_H} - V_{cc_L}$.

The P MOSFET transistor (BSP2220) is chosen with a breakdown voltage of -200 V to sustain the maximum voltage of the system.

In [Figure 2: "Typical application"](#) the voltage gain is set at 334.

3 Error analysis

We will now have a look at the precision of the "typical application" described in [Section 2: "Application"](#). Some inaccuracy exists and it is mainly due to the mismatch of the resistors and the offset of the amplifiers.

3.1 Impact of resistor mismatches

[Equation 1](#) gives a result of the output voltage by considering that the resistors are perfectly matched. Unfortunately, this is not the case, as the resistors have their own precision.

The error on the gain, due to the mismatch of the resistors, is given by [Equation 5](#).

Equation 5

$$V_0 = \frac{I_{sense} \cdot R_{shunt}}{R_1} \cdot \frac{R_4}{R_3} \cdot (R_1 + R_2 + R_3) \cdot \left[1 + \left(\frac{2R_1 + 4R_2 + 2R_3}{R_1 + R_2 + R_3} \right) \cdot \epsilon_\alpha + \epsilon_{R_{shunt}} \right]$$

Where ϵ_α is the precision of any of the resistors and $\epsilon_{R_{shunt}}$ is the accuracy of the shunt resistor. We can see that the R2 resistor has a bigger impact on the error than the other resistors. Consequently, its value must be as low as possible e.g. 10 k Ω is a good value for the TSZ121.

Considering [Figure 2: "Typical application"](#), if the resistors are chosen with a precision of 1 %, the gain error due to the mismatch will be 2.2 %. For better accuracy, resistors with a precision of 0.1 % should be chosen. In this case, the gain error will be 0.22 %.

Note that the error due to the shunt accuracy should be added (1 % on the shunt means 1 % more on the total error).

We need to keep the following points in mind:

- Choose R4 as high as possible to have a low I_{ds} current ([Equation 4](#))
- Choose R2 as low as possible to limit total error ([Equation 5](#))
- The sum of R1 and R3 should be high and unbalanced to achieve the gain required ([Equation 5](#)). Ideally, R1 should be low to limit the noise.

3.2 Impact of input voltage offset (V_{io})

The second error that must be taken into account is the input voltage offset (V_{io}). The TSZ121 is a chopper amplifier with a very low V_{io} , 8 μV over temperature. This error becomes important especially when a very small current has to be measured.

The transfer function, taking the V_{io} into account, can be written as shown below in [Equation 6](#).

Equation 6


$$V_{out} = \frac{(V_{sense} \pm V_{io1})}{R1} \cdot \frac{R4}{R3} \cdot (R1 + R2 + R3) \pm V_{io2}$$

Where V_{io1} is the input offset voltage of the first op amp (OP1) and V_{io2} is the input offset voltage of the second op amp (OP2).

As the TSZ121 has an extremely low input offset voltage, V_{io2} can be ignored.

[Figure 3](#) below shows the accuracy over temperature for a different V_{sense} voltage using the value shown in [Figure 2: "Typical application"](#).

Figure 3: Error on the output, with a different V_{sense} voltage, due to the V_{io}

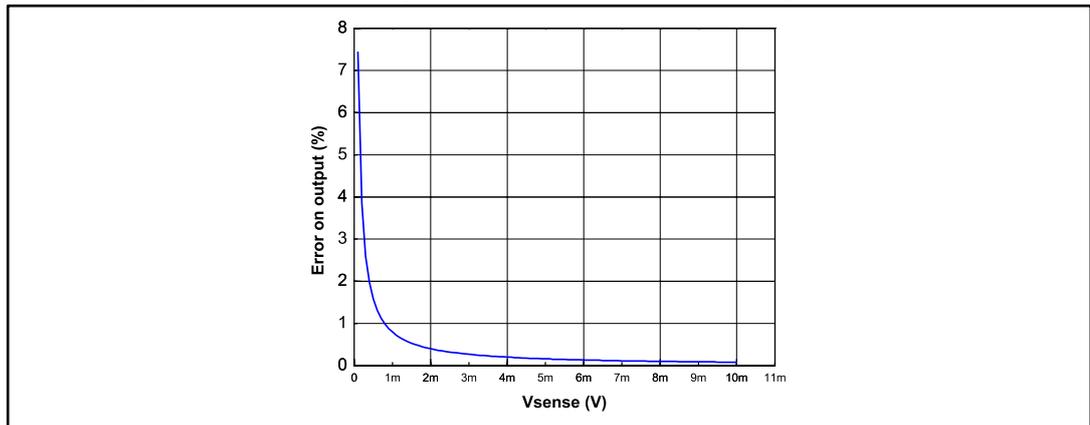

3.3 Total error


To get some idea of the total error on the output, we must add the error due to the mismatch of the resistors and the error due to the input voltage offset of the op amp. The output voltage can be written as shown in [Equation 7](#).

Equation 7


$$V0 = \frac{Isense \cdot Rshunt}{R1} \cdot \frac{R4}{R3} \cdot (R1 + R2 + R3) \cdot [1 + (\frac{2R1 + 4R2 + 2R3}{R1 + R2 + R3}) \cdot \epsilon\alpha + \epsilon Rshunt] \pm \frac{Vio}{R1} \cdot \frac{R4}{R3} \cdot (R1 + R2 + R3)$$

In the figures below, we see the percentage error on the output depending on the current flowing through the shunt resistor when we use resistors with a precision of 1 % or 0.1 % respectively.

[Figure 4](#) and [Figure 5](#) represent the maximum error expected over temperature without taking the shunt accuracy into account.

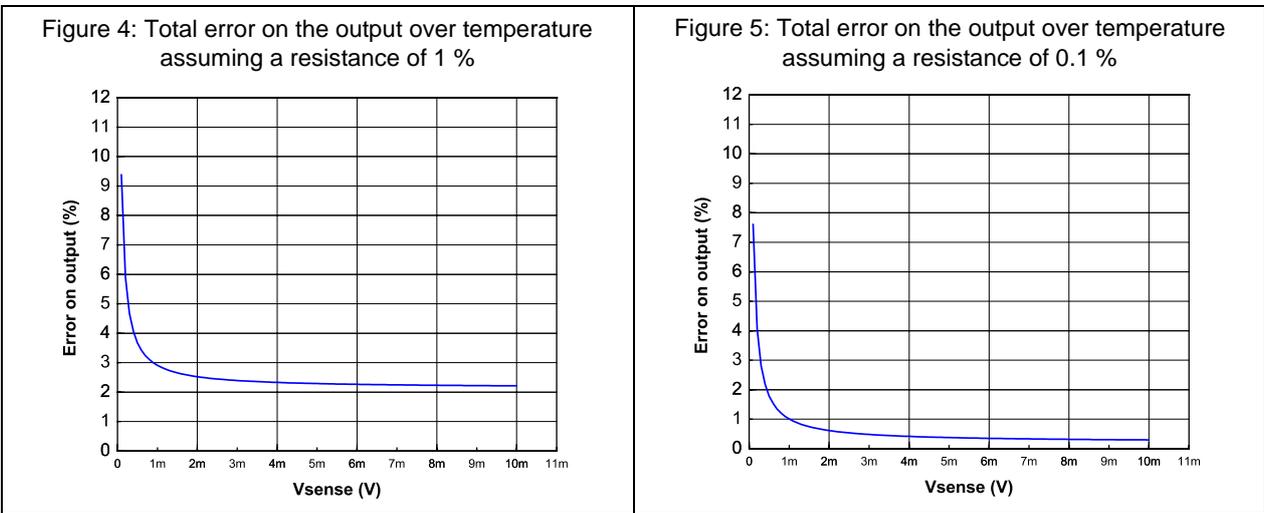

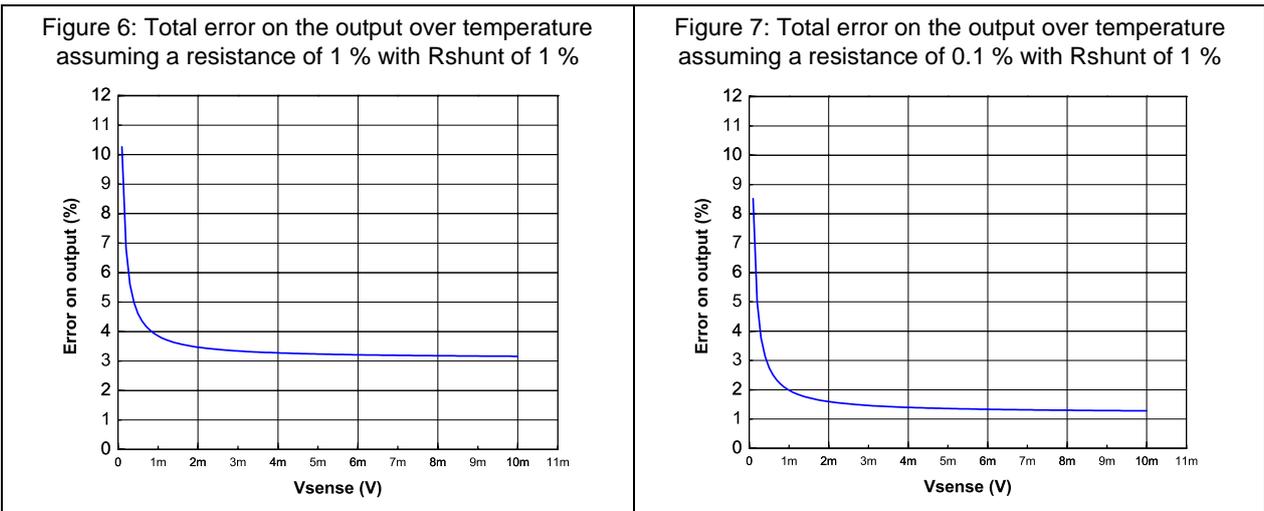[Figure 6](#) and [Figure 7](#) represent the maximum error expected over temperature when we take the shunt accuracy into account.




4 Application measurement

Figure 8 below shows the results of application board measurements made with the respect to the schematics of Figure 2: "Typical application". Resistances of 1 % precision were used. V_{sense} varies from 1 mV to 10 mV.

This measurement does not take into account the shunt accuracy.

Figure 8: Error on the output vs. V_{sense} at 25 °C

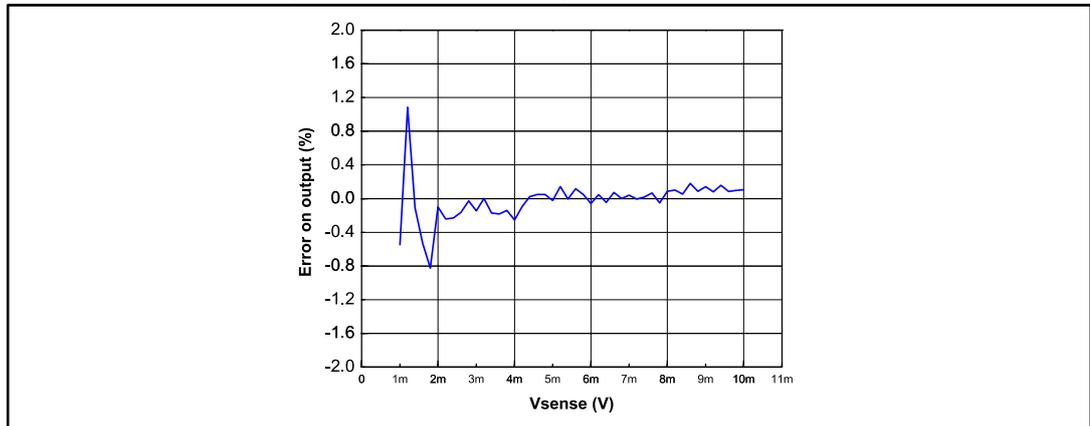

5 Conclusion

To realize high-side current sensing measurements, some dedicated circuits of the TSC10x family amplifier are commonly used. But, in applications where the common-mode voltage is higher than 70 V this kind of measurement should be done with a conventional 5 V op amp.

Effectively high-side current sensing can be achieved using a TSZ121 which is a low-voltage, precision amplifier. It is combined with a zener diode to work in a 5 V range and a level shift transistor.

Errors due to the resistors and amplifiers used must be taken into account. To obtain good accuracy for the current measurement it is advised to use 0.1 % precision resistors.

6 Revision history

Table 1: Document revision history

Date	Revision	Changes
21-Nov-2016	1	Initial release

IMPORTANT NOTICE – PLEASE READ CAREFULLY

STMicroelectronics NV and its subsidiaries (“ST”) reserve the right to make changes, corrections, enhancements, modifications, and improvements to ST products and/or to this document at any time without notice. Purchasers should obtain the latest relevant information on ST products before placing orders. ST products are sold pursuant to ST’s terms and conditions of sale in place at the time of order acknowledgement.

Purchasers are solely responsible for the choice, selection, and use of ST products and ST assumes no liability for application assistance or the design of Purchasers’ products.

No license, express or implied, to any intellectual property right is granted by ST herein.

Resale of ST products with provisions different from the information set forth herein shall void any warranty granted by ST for such product.

ST and the ST logo are trademarks of ST. All other product or service names are the property of their respective owners.

Information in this document supersedes and replaces information previously supplied in any prior versions of this document.

© 2016 STMicroelectronics – All rights reserved